

# HKN ECE 110 Review Session Exam 1

COREY SNYDER

STEVEN KOLACZKOWSKI

---

# What is charge? Current? Voltage? Resistance?

---

- Electrons carry charge and thus convey electrical energy
  - Units: Coulombs [C]
- Current is the flow of charge
  - Units: Coulombs/second = Amps [A] (Amperes)
- Voltage is the work done per unit charge. Think of this as the force or pressure on the electrons
  - Units: Joules/ Coulomb = Volts [V]
- Resistance is the opposition to the flow of charge
  - Units: Ohms [ $\Omega$ ]

# Energy vs. Power

---

- Energy is the ability to do work
  - Units: Joules [J]
- Energy can take on many forms
  - Potential Energy – Chemical, Electrical, Mechanical
  - Kinetic Energy
- Energy is always conserved!
- Power is the rate at which energy is transferred
  - Units: Joules/second = Watts [W]

# Capacitors

---

- A capacitor is a device that stores charge
  - Units: Coulombs/Volt = Farads [F]
  - This charge is said to be “coupled”

- $E_{\text{capacitor}} = \frac{1}{2} CV^2$

- $C = \frac{Q}{V}$

# Ohm's Law, Resistance, and Power

---

- Ohm's Law describes the relationship between the voltage *across* and current *through* a resistive element
  - Ohm's law only applies for linear components, i.e. resistors
  - More on linear components with Thevenin/Norton Equivalents (and in ECE 210!)
- $V = IR$
- Resistance of an element can be found by:  $R = \frac{\rho l}{A}$
- Power dissipated by an element can be found by:  $P = IV, P = I^2R, P = \frac{V^2}{R}$ 
  - You can go between the three forms using Ohm's Law!

# Nodes, KVL, and KCL

- A node is any part of a circuit that is at an *equipotential*

- Wires are equipotentials

- Kirchhoff's Voltage Law


- Conservation of Energy
- Performed on a loop

- $\sum V_{rises} = \sum V_{drops}$

- Kirchhoff's Current Law

- Conservation of Charge
- Performed at a node
- Bubble method


- $\sum I_{in} = \sum I_{out}$

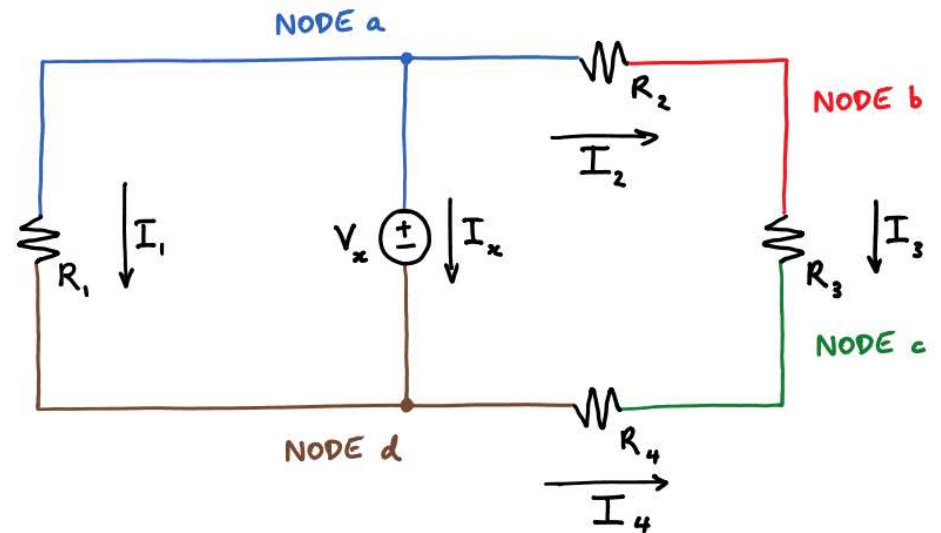
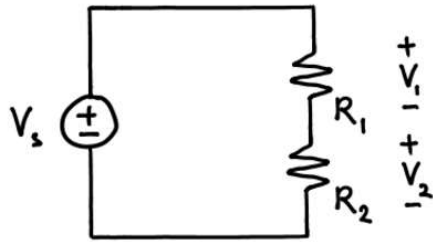
# Voltage Divider and Current Divider


---

- We can use voltage divider rule (VDR) in order to find the voltage across individual resistors in series



$$V_1 = \frac{R_1}{R_1 + R_2} V_s \quad V_2 = \frac{R_2}{R_1 + R_2} V_s$$

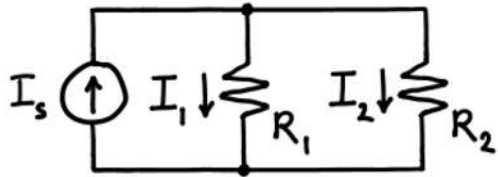- We can use current divider rule (CDR) in order to find the current through individual resistors in parallel



$$I_1 = \frac{R_2}{R_1 + R_2} I_s \quad I_2 = \frac{R_1}{R_1 + R_2} I_s$$

# Root-mean-square Voltage ( $V_{rms}$ )

---

- The exact definition of  $V_{rms}$  is:

$$V_{rms} = \sqrt{\frac{\left(\int_0^T f^2(t) dt\right)}{T}}$$

- We will mainly ask you to use the following two formulas:

- $V_{rms}(\text{sinusoid}) = \frac{\text{Amplitude}}{\sqrt{2}}$

- $V_{rms}(\text{square wave}) = V_{p-p} \sqrt{\%DC}$

- We use  $V_{rms}$  to determine the power delivered to a load from a time-varying source



- $P_{avg} = \frac{V_{rms}^2}{R}$


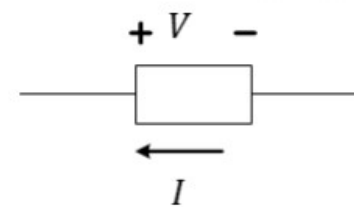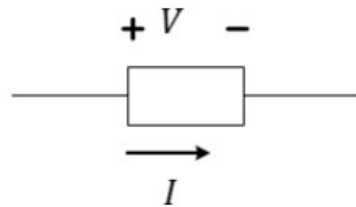
# Power and Labeling

---

- We know that power can be expressed in three ways:  $P = IV = I^2R = \frac{V^2}{R}$
- If the value of power is positive, the element is absorbing power
- If the value of power is negative, the element is supplying power
- Standard vs. Non-Standard Labeling
- Standard:  $P = IV$ ,  $V = IR$ , Current goes + to -
- Non-Standard:  $P = -IV$ ,  $V = -IR$ , Current goes - to +



# I-V Characteristics

---

- We can characterize circuits where the current is a function of the voltage
- For ECE 110, we typically want to characterize linear circuits, where the I-V Characteristic is of the form
  - $I = mV + b$
- In order to obtain this equation, we want to find two points:
  - $V_{oc}$  and  $I_{sc}$
- $V_{oc}$  is the  $x$  – intercept,  $I_{sc}$  is the  $y$  – intercept

# Legit Tips and Tricks to Show Off Your Wits

---

- Use your note sheet more like a study tool
- Use the practice exam on PrairieLearn
- Do not spend too much time on questions you cannot answer
- Spend your time showing what you know
- Study past exams