 


ECE120 Midterm 2


HKN Review Session



CMOS

CMOS means Complementary Metal-Oxide-Semiconductor Transistor.

 
CMOS circuit contains PMOS transistor and NMOS transistor.



NMOS & PMOS


- In a NMOS, carriers are electrons
- When a high voltage is applied to the gate, NMOS will conduct
- In a PMOS, carriers are holes.
- When a high voltage is applied to the gate, PMOS will not conduct
- Parallel and series duality.

Practice

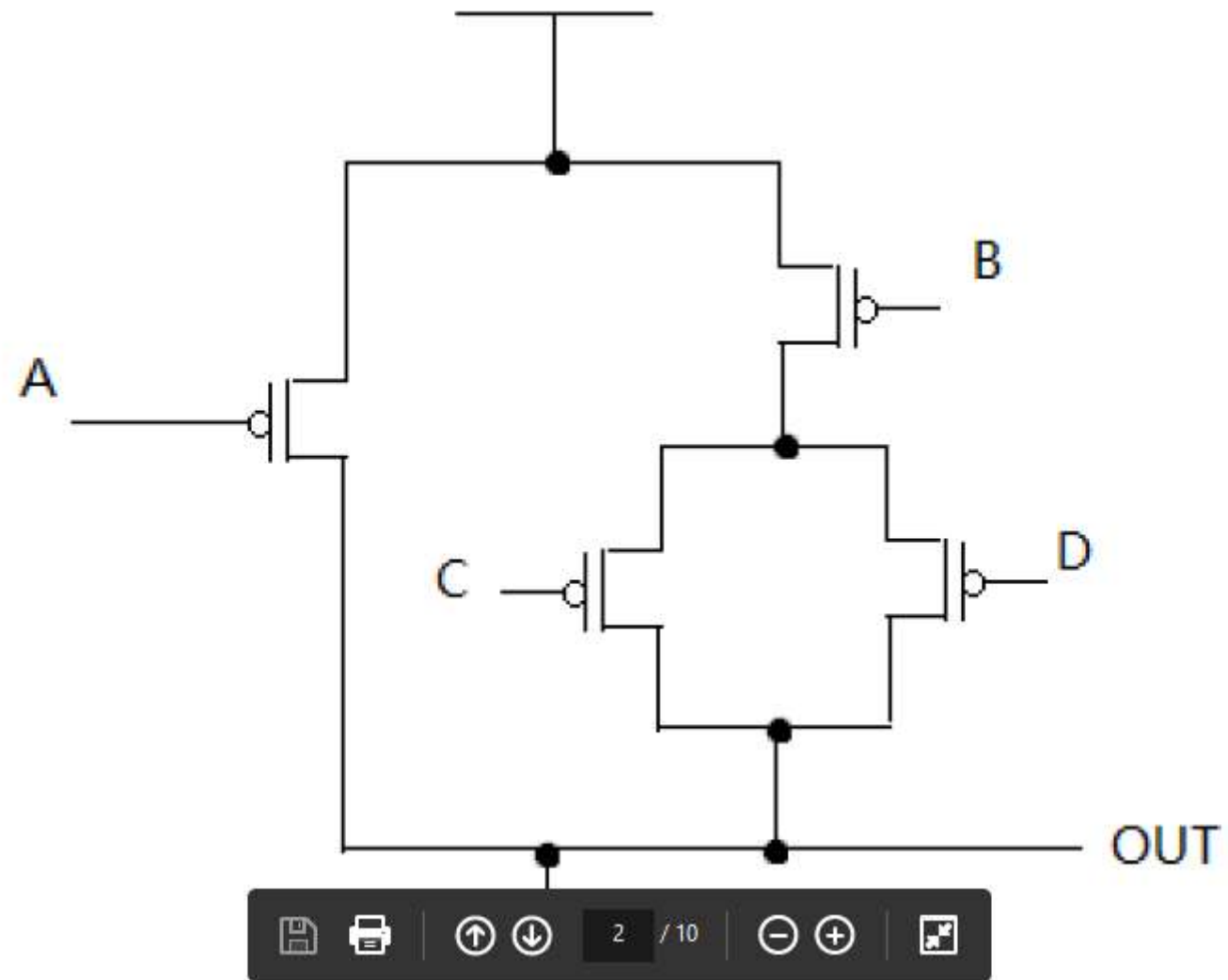

Karnaugh maps

 - Gray code order: to put adjacent cells together
- Minimal expression can be derived by grouping neighboring cells into powers of 2



- Implicant—a rectangular cover of 1's or X's
- Prime implicant—an implicant (containing at least one minterm) that is not wholly covered by a single other implicant
- Essential prime implicant—a prime implicant containing a minterm that is not covered by another prime implicant
- $|\text{Non-essential PI}| + |\text{Essential PI}| = |\text{PI}|$

- Cover the remaining 1's using as few prime implicants as possible
- In other words, find minimum number of rectangles to cover all 1's in K-map, each rectangle as large as possible

Minterms(1) and Maxterms(0)

Capitalize M for maxterm and lowercase m for minterm (have this table on your sheet)

Variable			Minterm		Maxterm	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x+y+z$	M_0
0	0	1	$x'y'z$	m_1	$x+y+z'$	M_1
0	1	0	$x'yz'$	m_2	$x+y'+z$	M_2
0	1	1	$x'yz$	m_3	$x+y'+z'$	M_3
1	0	0	$xy'z'$	m_4	$x'+y+z$	M_4
1	0	1	$xy'z$	m_5	$x'+y+z'$	M_5
1	1	0	xyz'	m_6	$x'+y'+z$	M_6
1	1	1	xyz	m_7	$x'+y'+z'$	M_7

Boolean Algebra Properties

- Suppose a and b are literals. Then, $a \cdot b$ as well as ab reads “ a AND b ”, $a+b$ reads “ a OR b ”, a' reads “NOT a ” (same as \bar{a})
- Writing truth tables
- POS: $(a+b) \cdot (x'+y)$
 - Circle all rows where $f(x, y, \dots) = 0$
- SOP: $ab+x'y+abxy$
 - Circle all rows where $f(x, y, \dots) = 1$

Proof: exhaustion or find a counter example.

- POS to SOP:

$$(A+B)(C+D+E) = AC+AD+AE+BC+BD+BE$$

- SOP to POS:

- use Boolean algebra distributivity property:

$$A+BC=(A+B)(A+C)$$

- Example:

$$wx'+y+vz$$

$$= (w+y)(x'+y)+vz$$

$$= [(w+y)(x'+y)+v][(w+y)(x'+y)+z]$$

$$= (w+y+v)(x'+y+v)(w+y+z)(x'+y+z)$$

Canonical forms

- Boolean function expressed as a sum of minterms is termed the *canonical sum of products* form of the function

- Example:

$$\begin{aligned}f &= x'y'z' + x'y'z + x'yz' + x'yz + xyz' \\ &= m_0 + m_1 + m_2 + m_3 + m_6 \\ &= \Sigma(m_0, m_1, m_2, m_3, m_6)\end{aligned}$$

- Boolean function expressed as a product of maxterms is termed the *canonical product of sum* form of the function
- Example:
$$f = (x' + y + z)(x' + y + z')(x' + y' + z')$$
$$= M4 \ M5 \ M7$$
$$= \Pi(M4, M5, M7)$$
- JUST a binary to decimal
- Max = 0, Min = 1

Don't Cares

- Implicants can include Don't cares but cannot be made up of only don't cares.
- Use don't cares to make your SOP or POS simpler. Include them only when it reduces the SOP/POS expression.

CD \ AB	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	d	1	0	d
10	d	d	d	d



SOP/POS to CMOS

- SOP \Rightarrow AND/OR
- AND/OR \Rightarrow NAND
- Example: $F = A'B + BC + D$

- POS \Rightarrow OR/AND
- OR/AND \Rightarrow NOR
- Example: $F = (A + B + C')(A + C)(B')$




Bit-Slice Design

 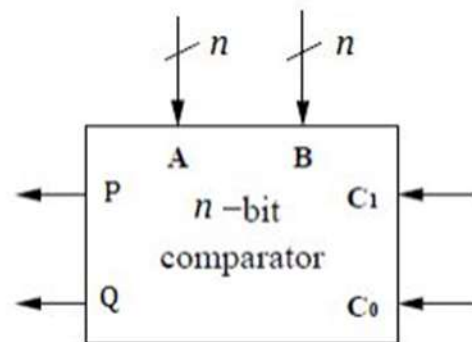- Comparator has two outputs
 - Represent $A=B$, $A>B$, $A<B$ (4th comb. unused)
- Adder produces sum bit and carry bit




MUX

2^n inputs for n select bits

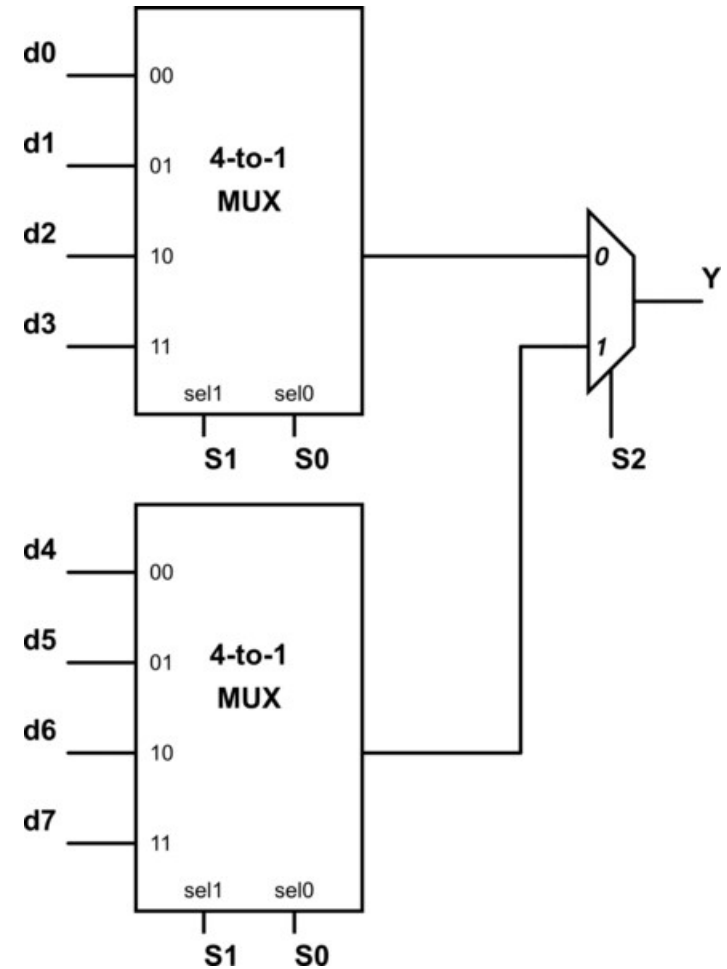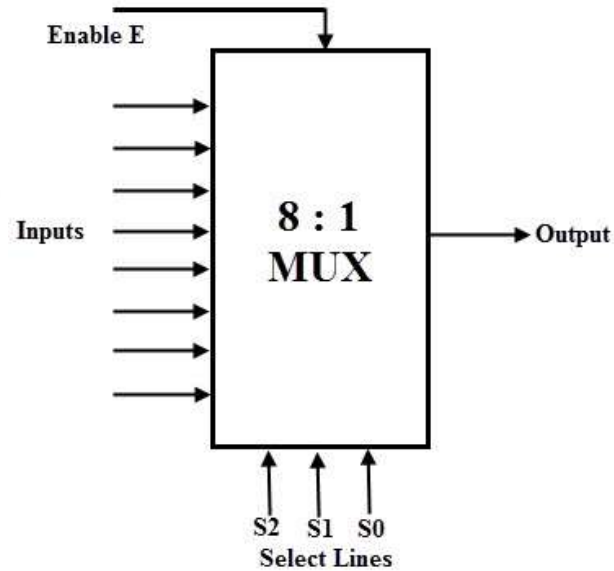 

Decoders

 - Decoder is a minterm generator. Any n -variable function can be implemented using a 2^n decoder and a single OR gate.
- n inputs 2^n outputs.




Combinational and Sequential Logic

- Combinational circuit: Output is a function of its input **ONLY**
- Sequential circuit: Depends on the current and past inputs.


Latches

■ SR Latch

 

S	R	Q ⁺
0	0	Q (hold)
0	1	0 (reset)
1	0	1 (set)
1	1	forbidden

■ D Latch

 



C	D	R	S	Q ⁺	
1	0	1	0	0	reset
1	1	0	1	1	set
0	0	0	0	Q	no change
0	1	0	0	Q	no change

Flip-flops

■ D flip-flop

D flip-flop

D	Q+
0	0
1	1

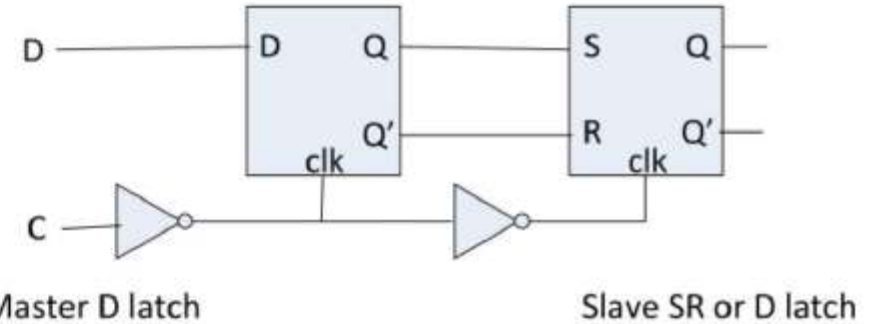 


Changes happens only on the edges of clock (positive edge or negative edge)

■ Other kinds of flip-flops: T, SR, JK....


Registers

It seems like a group of flip-flops

- **Logical Shift Right:**

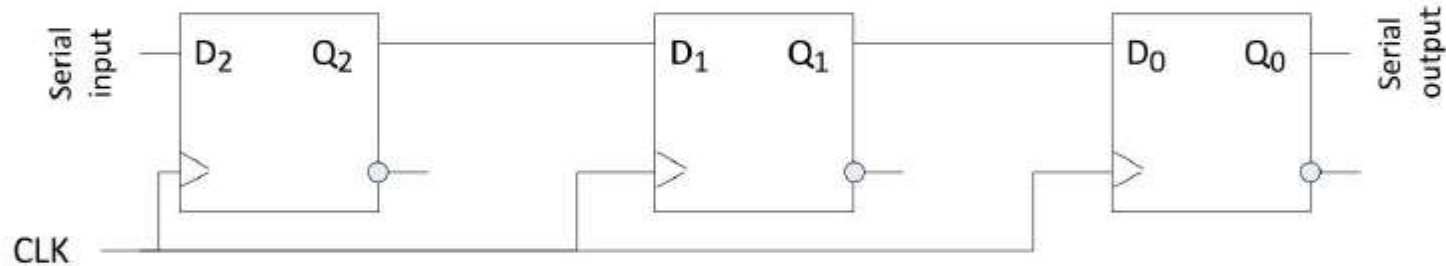


- **Logical Shift Left:**

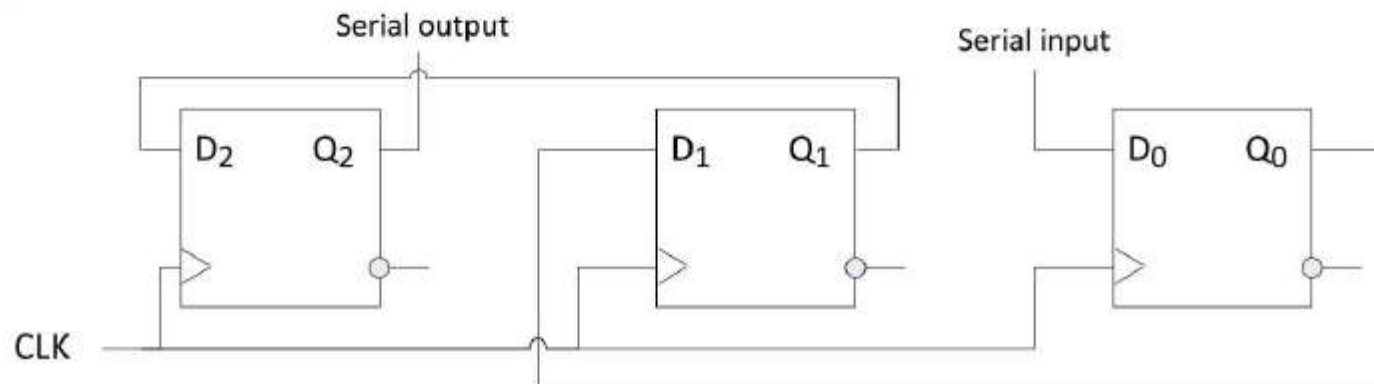


Registers

■ Circular Shift Left:

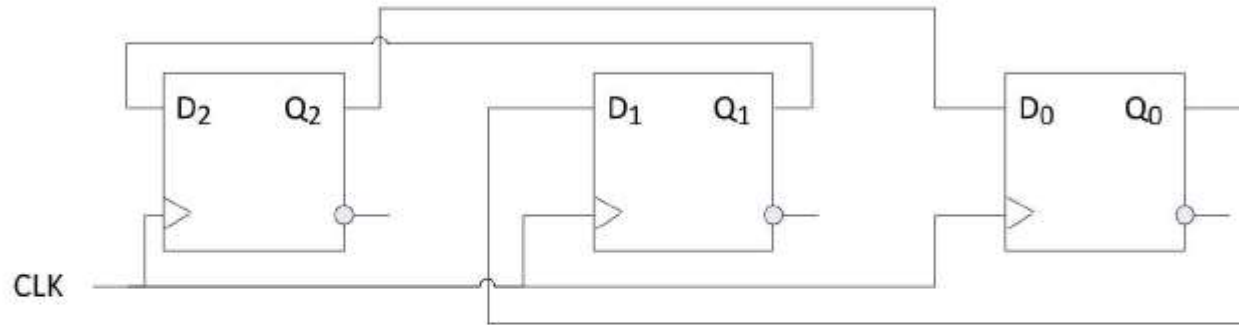


■ Circular Shift Right:

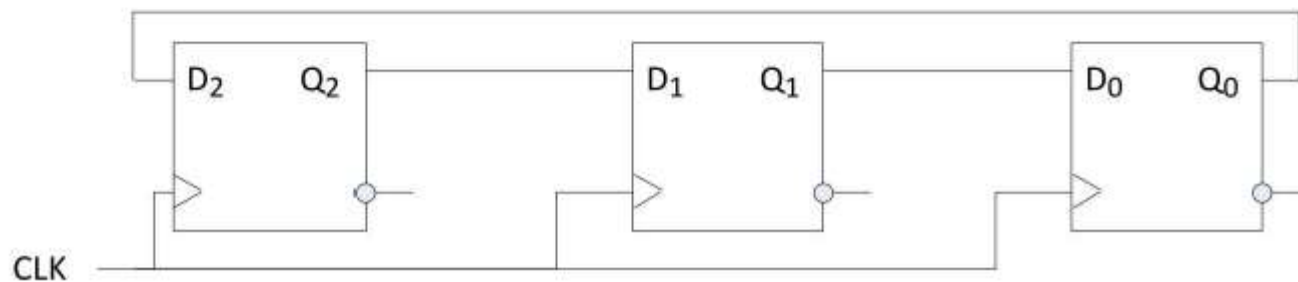

Registers

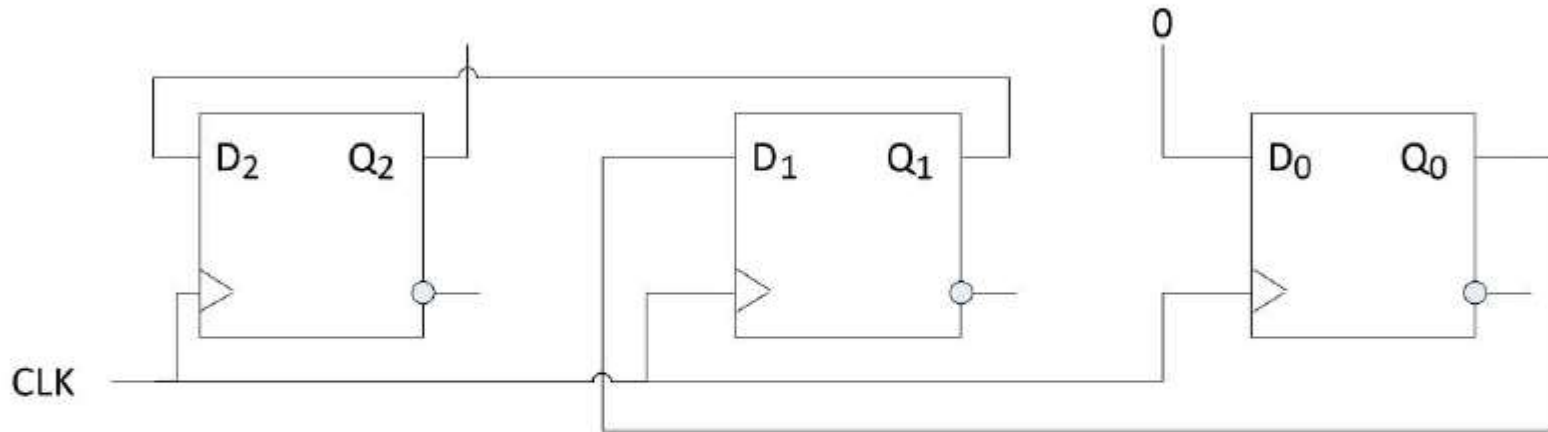- **Arithmetic Shift Left: Must shift in 0**



- **Arithmetic Shift Right: Can't change sign bit**

