

ECE 210
Exam 1 Review Session

HKN

Today's agenda

- Key concepts (with examples)
- Fall 2015 Practice Exam
- Spring 2016 Practice Exam (if time allows)


Circuit Fundamentals

Electrical Circuits


Components



Resistor

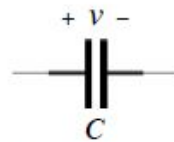

Capacitor

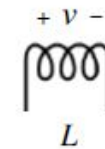





Inductor

Ohm's Law

$$v = iR$$

Electrical Circuits

Sources

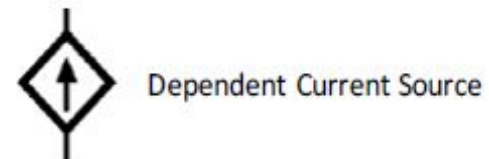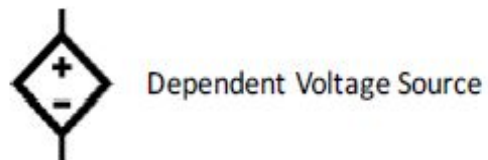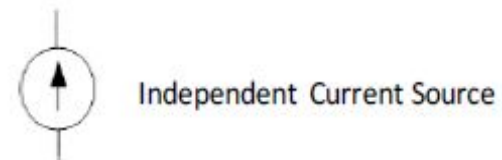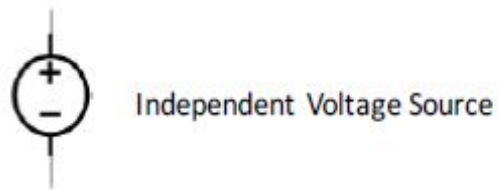

Power Absorption vs. Delivery

- $P = V * I$

V - voltage drop (defined vs. actual)

I - current along the direction of voltage drop

- $P > 0$ - absorb power

$P < 0$ - deliver power

Kirchhoff's Voltage & Current Law

Kirchhoff's Voltage Law (KVL)


$$\sum_{all\ k} V_i = 0, \text{ around a loop}$$

Kirchhoff's Current Law (KCL)

$$\sum_{all\ k} I_k = 0, \text{ at a node}$$

Spring 2015 Exam 1

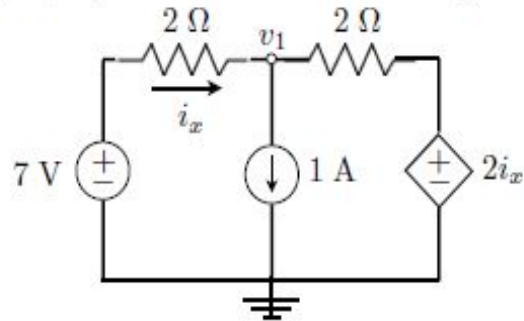3. (13 pts) Consider the following circuit:



(a) (3 pts) Write a single equation expressing the current i_x in terms of the node voltage v_1 .

(b) (8 pts) Find the node voltage v_1 and the current i_x .

$$v_1 = \underline{\hspace{2cm}}$$

$$i_x = \underline{\hspace{2cm}}$$

(c) (2 pts) **TRUE** or **FALSE**: The dependent voltage source is delivering power to the circuit. Justify your answer by indicating the direction of *positive* current through it on the diagram.

Complex Numbers

Rectangular Form

$$z = a + jb, \text{ where } j = \sqrt{-1} \text{ and } a, b \in \mathbb{R}$$

Polar Form

$$z = Ae^{j\phi} = A\angle\phi, \text{ where } A = |z| \text{ and } \phi = \angle z$$

Rectangular Form \leftrightarrow Polar Form

$$A = |z| = \sqrt{a^2 + b^2} \quad \phi = \angle z = \begin{cases} \tan^{-1}\left(\frac{b}{a}\right), a \geq 0 \\ \tan^{-1}\left(\frac{b}{a}\right) + \pi, a < 0 \end{cases}$$

Complex Numbers

Euler's Identity

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

2. (12 pts) Obtain the real and imaginary parts of Z , as well as its magnitude and phase.

$$Z = \left(\frac{j}{e^{j\frac{\pi}{3}}} - e^{-j\frac{\pi}{6}} \right) e^{j\frac{\pi}{4}}$$

Spring 2015 Exam 1

$$R_e \{Z\} = \underline{\hspace{2cm}}$$

$$I_m \{Z\} = \underline{\hspace{2cm}}$$


$$|Z| = \underline{\hspace{2cm}}$$

$$\angle Z = \underline{\hspace{2cm}}$$

Resistor Combinations


Series Combination
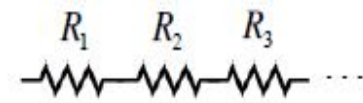
$$R_{eq} = \sum_i R_i = R_1 + R_2 + \dots$$



Parallel Combination

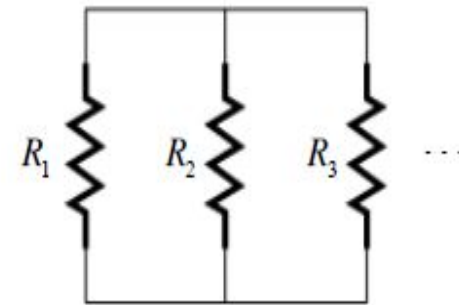
$$\frac{1}{R_{eq}} = \sum_i \frac{1}{R_i} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$



Resistor Combinations


Voltage Divider Rule
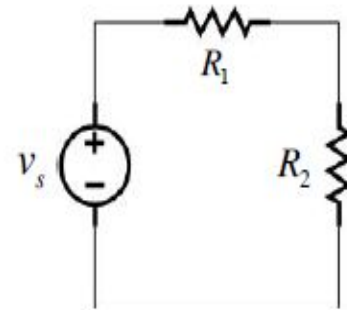
$$v_1 = v_s \frac{R_2}{R_1 + R_2}, \quad v_2 = v_s \frac{R_1}{R_1 + R_2}$$




Current Divider Rule
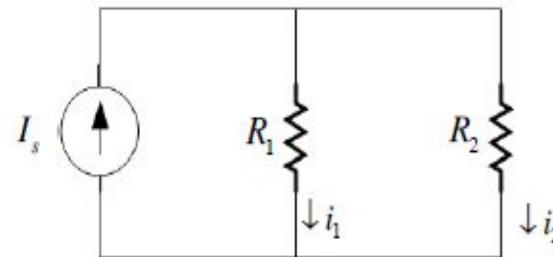
$$i_1 = I_s \frac{R_2}{R_1 + R_2}, \quad i_2 = I_s \frac{R_1}{R_1 + R_2}$$



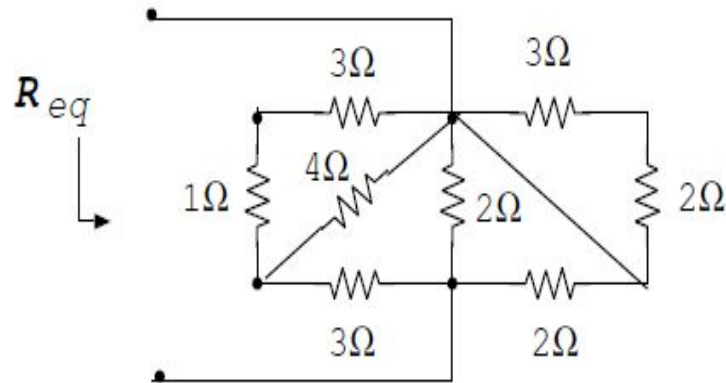(b) Find the equivalent resistance between terminals a and b in the circuit below.




$$R_{eq} = \underline{\hspace{2cm}}$$


Fall 2014 Exam 1 Problem 1(b)

Source Combinations

Voltage Source

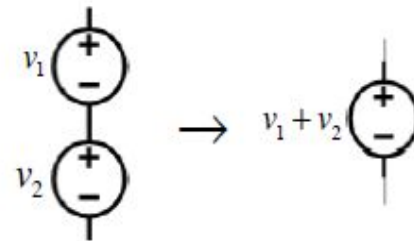

Current Source

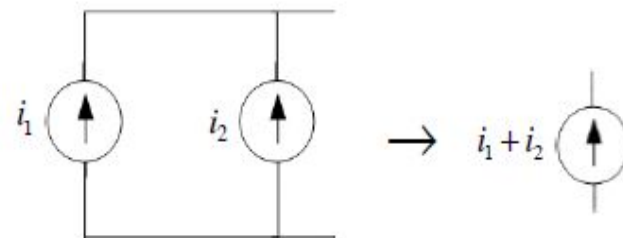

Questions?